

GREENHILL ACADEMY-SECONDARY.

TERM 3 HOLIDAY WORK

S.5 PHYSICS 2 (P510/2)


Answer **all** questions.

Assume where necessary the following constants;

✓ Acceleration due to gravity, g	=	9.81ms^{-2}
✓ Electron charge, e	=	$1.6\times 10^{-19}\text{C}$
✓ Electron mass	=	$9.11\times 10^{-31}\text{kg}$
✓ Speed of light in a vacuum, c	=	$3.0\times 10^8\text{ms}^{-1}$
✓ Permittivity of free space ϵ_0	=	$8.85 \times 10^{-12} \text{Fm}^{-1}$
✓ The constant $\frac{1}{4\pi\epsilon_0}$	=	$9.0 \times 10^9 \text{F}^{-1}\text{m}$

DIRECT CURRENT (20 marks)

- A battery of e.m.f 12v and internal resistance 2Ω is connected to a wire of resistance 10Ω
 - calculate the p.d across the wire (3 marks)
 - what will be the p.d across the wire when a 15Ω resistor is connected in parallel with it? (4 marks)
- Explain how a moving coil galvanometer which has resistance of 25Ω and full scale deflection of 4.0mA can be converted to an ammeter reading a maximum of 1A . (3 marks)
- In the circuit below V is a voltmeter of resistance 600Ω

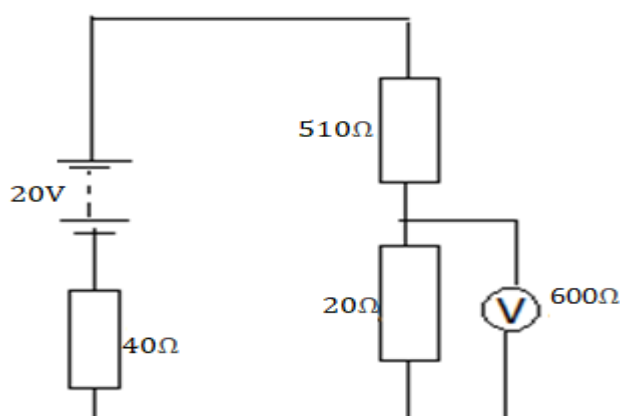


- find the reading of the voltmeter (3 marks)
 - calculate the power dissipated in the 40Ω resistor (2 marks)
- A battery of e.m.f 90V and negligible internal resistance is connected in series with a 600Ω and a 400Ω resistor. A voltmeter connected across the 600Ω resistor reads 45V. Determine the resistance of the voltmeter. (5marks)

CAPACITORS (15 marks)

5. A voltage of 100V is applied across the plates of a parallel plates capacitor whose plates are of dimensions 15 cm by 12 cm separated by an insulator of thickness 8mm and relative permittivity 2.3.
- (i) Determine the capacitance of the capacitor. (3 marks)
 - (ii) Calculate the charge stored by the capacitor (3 marks)
6. Two identical parallel plates capacitors of capacitance C are connected in series across a source of p.d V . A dielectric of relative permittivity, ϵ_r is inserted in one of the capacitors;
- (i) Determine the effective capacitance of the capacitors. (3 marks)
 - (ii) Determine the energy stored in the network before and after the dielectric is inserted. Hence Show that the energy stored increases by a factor of $\frac{2\epsilon_r}{(1 + \epsilon_r)}$ (6 marks)

ELECTROSTATICS (15 marks)

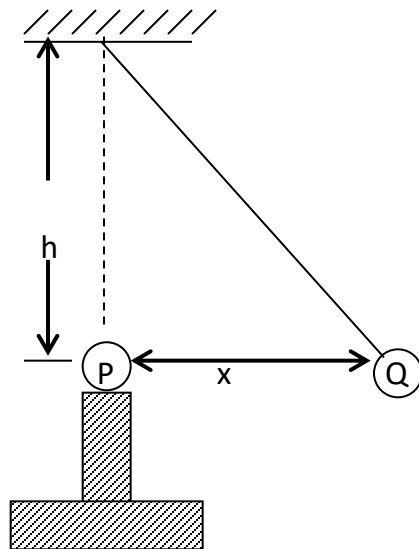
7. The figure below shows two identical metal balls P and Q of mass m , arranged in air with P fixed on an insulating stand and Q suspended by a silk thread from a height h , above P.



When the balls are given identical charge q they repel. In equilibrium, the balls are at a distance x apart as shown in the diagram above.

- (i) Show that the charge $q = \sqrt{\frac{4\pi\epsilon_0 mgx^3}{h}}$ (4 marks)
- (ii) Sketch the electric field pattern between the charges P and Q (2 marks)

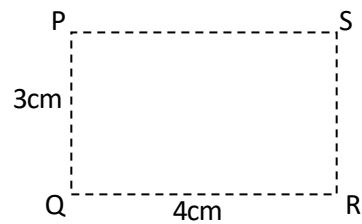8. Charges of $-3\mu\text{C}$, $+4\mu\text{C}$ and $+3\mu\text{C}$ are placed at the corners P, Q and R of a rectangle PQRS in which $PQ = 3\text{ cm}$ and $QR = 4\text{ cm}$ as shown in the figure below



- (i) If the charges are in vacuum, calculate the electric intensity at S. (7 marks)
- (ii) Sketch the electric field pattern for the above charge distribution. (2 marks)

END